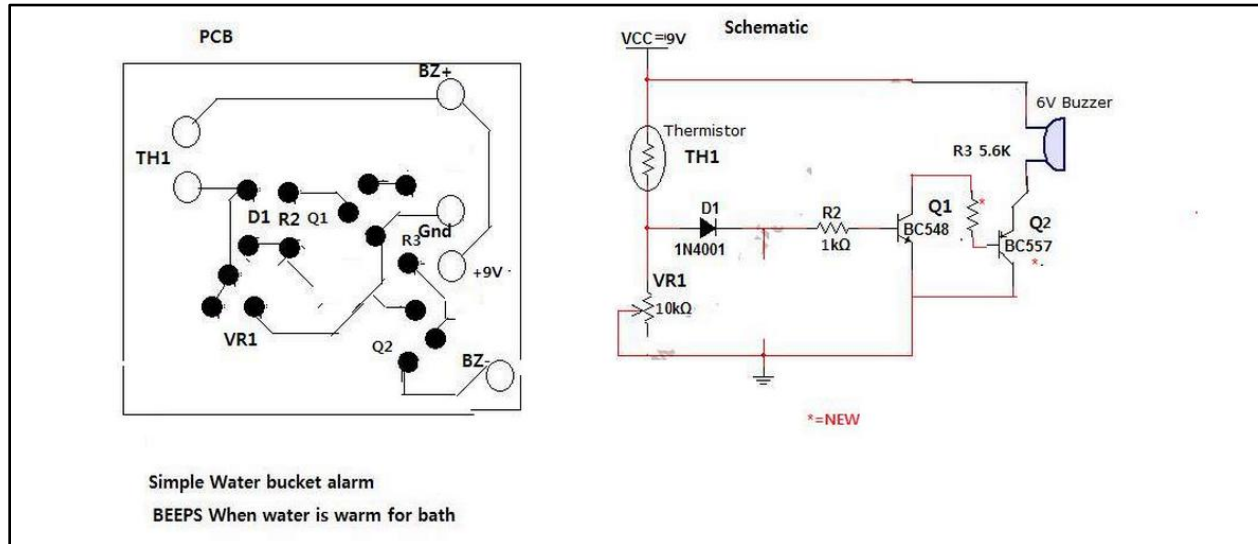


BATH BUCKET ALARM TESTED VERSION VERY SIMPLE-version1

=====

বাকেত ত পানী গৰম কৰিলে ই সময়ত বিপ দিয়ে

So tested the circuit simple circuit no zener , just 2 transistors
it is working nicely



Cost 50Rs for parts

Parts List

Transistor

PNP BC557

NPN BC547

1N4007 [pull from old circuits] ,

1K,5.6k ,[if not preset 2.2K,820ohms] 1/4watt

10K thermistor , 10K preset ,board some wires,9v battery etc

Version2 eta water sensor loguwaase to eliminate ON/off

DIP KORILEI ON HOBO

