 


AND-OR


An AND-OR circuit directly implements an SOP expression



AND-OR-INVERT LOGIC


$$X = (\bar{A} + \bar{B})(\bar{C} + \bar{D}) = (\bar{A}\bar{B})(\bar{C}\bar{D}) = \overline{(\overline{\bar{A}\bar{B}})\overline{\bar{C}\bar{D}}} = \overline{AB + CD} = \overline{AB} + \overline{CD}$$

 When the output of an AND-OR circuit is complemented (inverted), it results in an AND-OR Invert circuit.



EXCLUSIVE-OR

 
Although this circuit is considered a type of logic gate with its own unique symbol, it is actually a combination of two AND gates, one OR gate, and two inverters.



EXCLUSIVE-NOR LOGIC

Notice that the output X is HIGH only when the two inputs, A and B, are at the same level.

 
$$X = \overline{A\oplus B} = (\overline{A\bar{B} + \bar{A}B}) = (\bar{A}\bar{B})(AB) = (\bar{A} + B)(A + \bar{B}) = \overline{A\bar{B} + B\bar{A}}$$



Two equivalent ways of implementing the exclusive-NOR.


EVEN-PARITY GENERATOR

 A parity bit is added to a binary code in order to provide error detection. For even parity, a parity bit is added to the original code to make the total number of 1s in the code even. The circuit in Figure 5-7 produces a 1 output when there is an odd number of 1s in the code even. A 0 output is produced when there is an even number of 1s on the inputs.



EVEN-PARITY CHECKER

 
Produces a 1 output when there is an error in the five-bit code and a 0 when there is no error.



FROM A BOOLEAN EXPRESSION TO A LOGIC CIRCUIT


Unless an intermediate term, such as CD + EF, is required as an output for some other purpose, it is usually best to reduce a circuit to its SOP form in order to reduce the overall propagation delay time. The expression is converted to SOP as follows:
 
$$A B C \bar{D} + E F = A B C \bar{D} + A B E F$$




FROM A TRUTH TABLE TO A LOGIC CIRCUIT

Inputs			Output	Product Term
A	B	C	X	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	$\bar{A}BC$
1	0	0	0	
1	0	1	0	
1	1	0	0	
1	1	1	0	

 

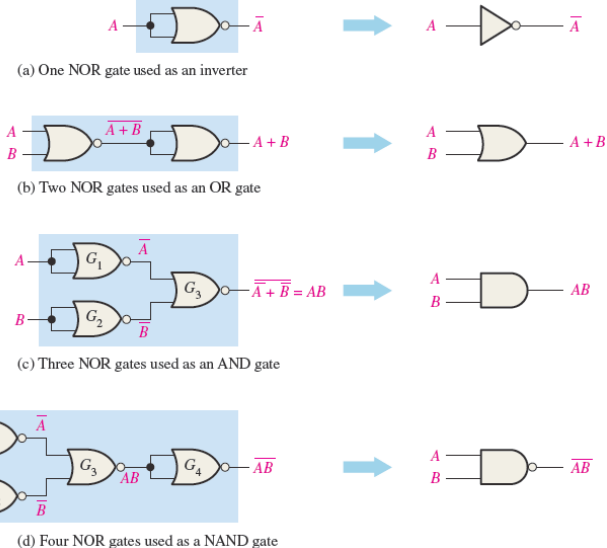THE NOR GATE AS A UNIVERSAL LOGIC ELEMENT



NAND LOGIC

As you have learned, a NAND gate can function as either a NAND or a negative-OR because, by DeMorgan's theorem,

$$\overline{AB} = \bar{A} + \bar{B}$$

NAND ↑ ↑ negative-OR

Consider the NAND logic in Figure 5-20. The output expression is developed in the following steps:

$$\begin{aligned} X &= \overline{(\overline{AB})(\overline{CD})} \\ &= \overline{(\bar{A} + \bar{B})(\bar{C} + \bar{D})} \\ &= \overline{(\bar{A} + \bar{B}) + (\bar{C} + \bar{D})} \\ &= \overline{\bar{A}\bar{B} + \bar{C}\bar{D}} \\ &= AB + CD \end{aligned}$$

 


FIGURE 5-20 NAND logic for $X = AB + CD$.

As you can see in Figure 5-20, the output expression, $AB + CD$, is in the form of two AND terms ORed together. This shows that gates G_2 and G_3 act as AND gates and that gate G_1 acts as an OR gate, as illustrated in Figure 5-21(a). This circuit is redrawn in part (b) with NAND symbols for gates G_2 and G_3 and a negative-OR symbol for gate G_1 .

Notice in Figure 5-21(b) the bubble-to-bubble connections between the outputs of gates G_2 and G_3 and the inputs of gate G_1 . Since a bubble represents an inversion, two

THE NAND GATE AS A UNIVERSAL ELEMENT


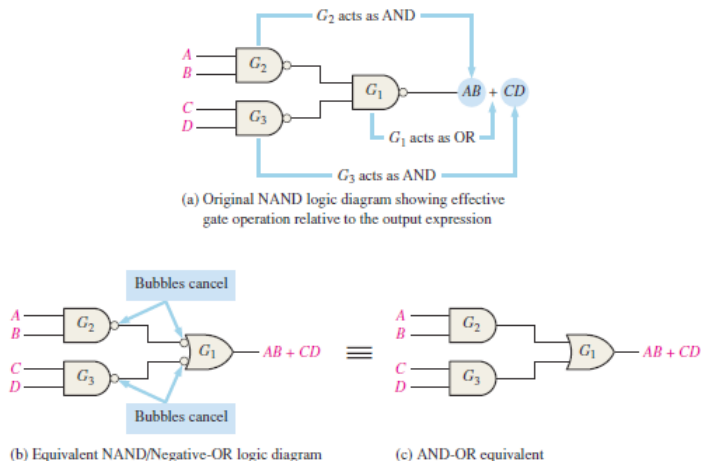
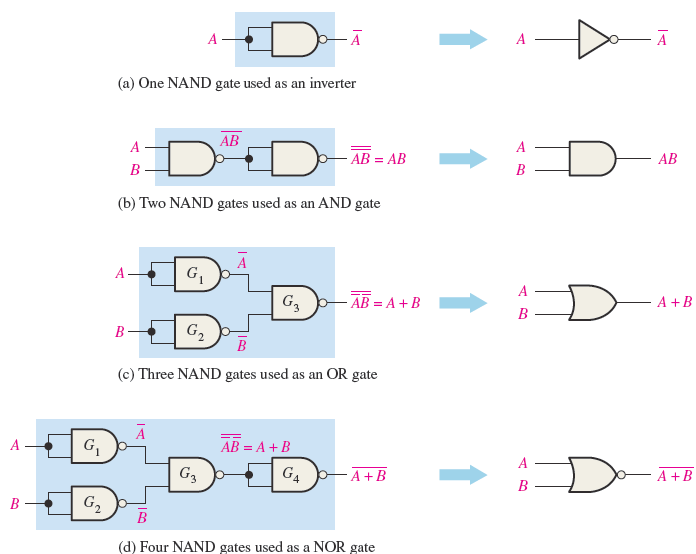



FIGURE 5-21 Development of the AND-OR equivalent of the circuit in Figure 5-20.

NAND LOGIC DIAGRAMS USING DUAL SYMBOLS

All logic diagrams using NAND gates should be drawn with each gate represented by either a NAND symbol or the equivalent negative-OR symbol to reflect the operation of the gate within the logic circuit. The NAND symbol and the negative-OR symbol are called dual symbols. When drawing a NAND logic diagram, always use the gate symbols in such a way that every connection between a gate output and a gate input is either bubble-to-bubble or nonbubble-to-nonbubble. In general, a bubble output should not be connected to a nonbubble input or vice versa in a logic diagram.

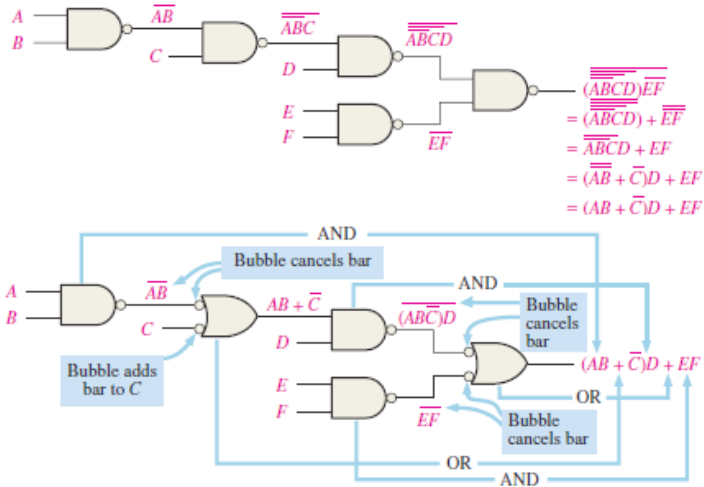

NAND USING DUAL SYMBOLS EXAMPLE PROBLEM

 

Redraw the logic diagram with the use of equivalent negative-OR symbols as shown. Writing the expression for X directly from the indicated logic operation of each gate gives:

